

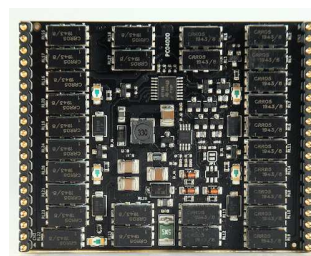


Product General Description


NanoPlex NPS-06-01-04A Universal Relay ISP-Channel Multiplier allows the expansion of the number of channels of ISP-Programming tools, while also offering galvanic isolation. The total number of switched signals is 24. NanoPlex is used on PCBAs production lines, in ATE-controlled ISP programming. Thanks to its ultra-small size (only 51.0x66.5 mm), NanoPlex takes easily place in Test Fixtures. Designed for piggyback mounting, NanoPlex is universal and compatible with all types of ISP Programming tools.

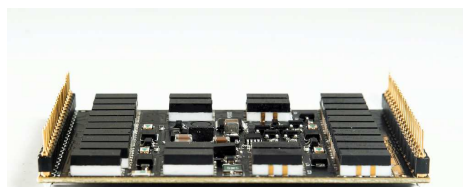

Block Diagram

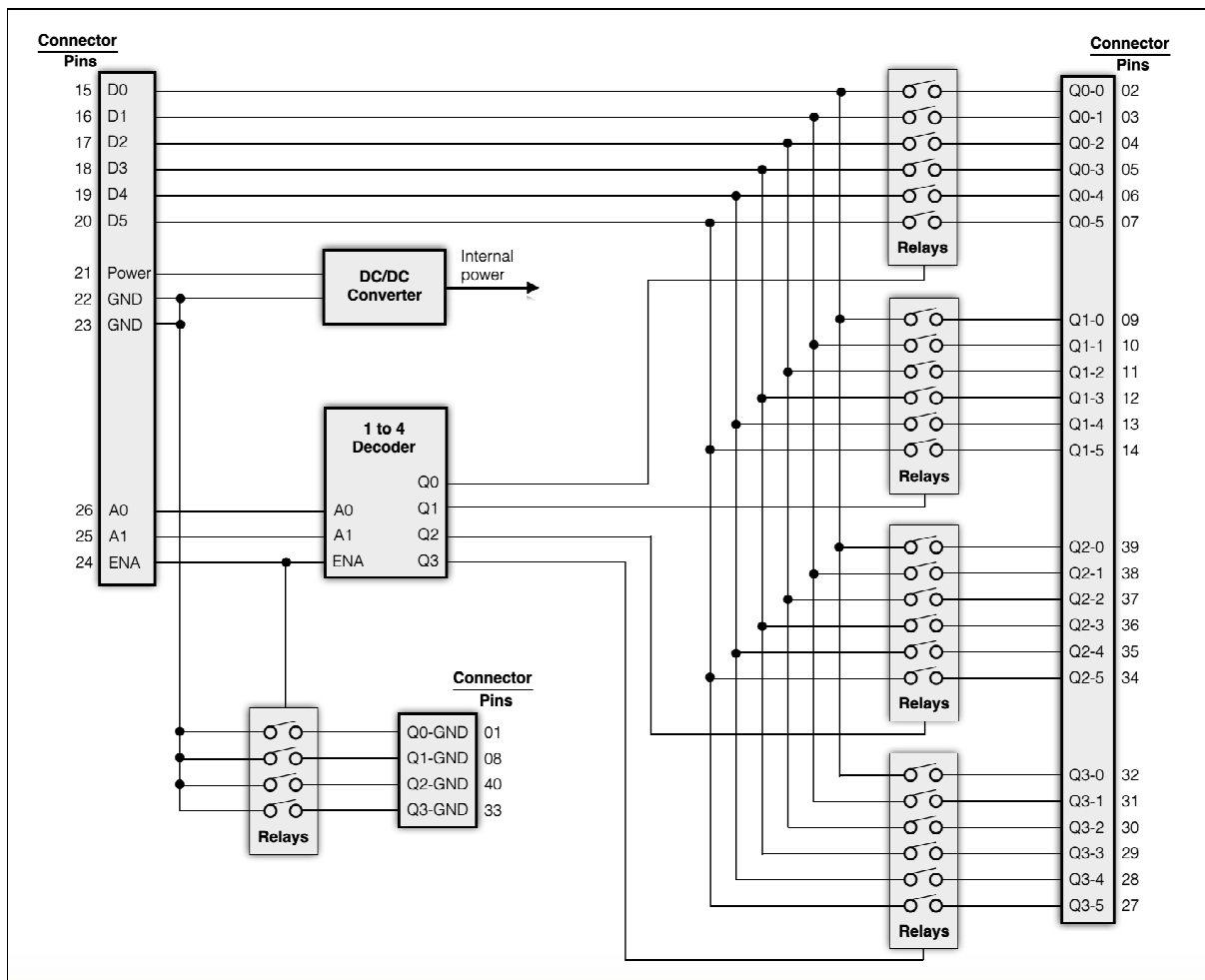

Layout (top view)

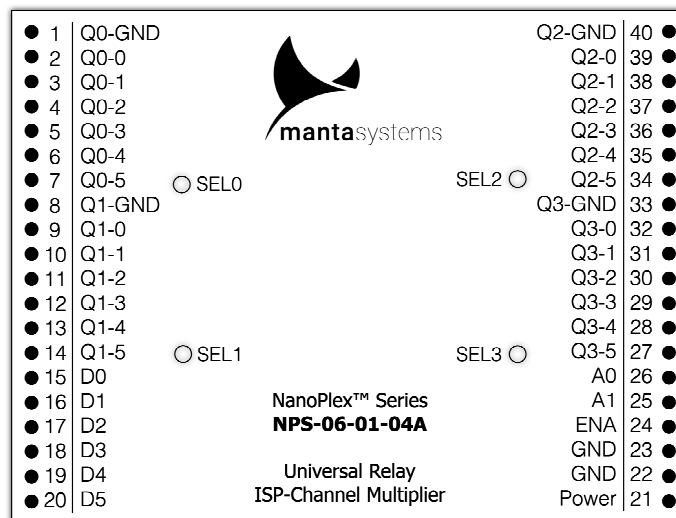

NPS-06-01-04A Operating Modes


Depending on the required number of signals per every channel, four operating modes are possible. On the following mode examples diagrams, for a better explanation of all the possible operating modes, signal names are assigned with aliases (texts are in **bold**).

Mode 1x4

6 Signals per channel

1 Input channel

4 Output channels

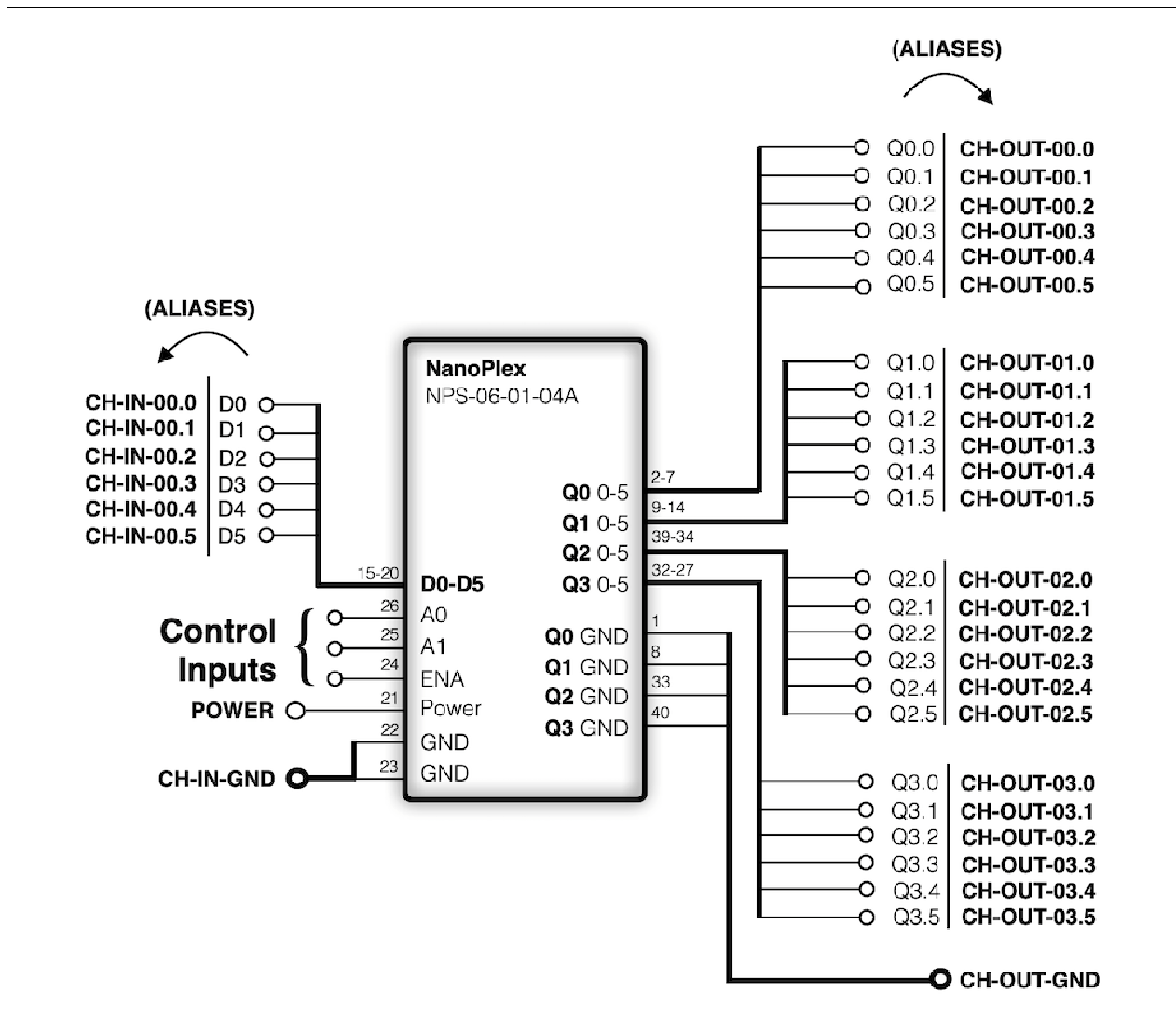

Truth table

(the symbol ► stands for “connected to”)

ENA	A1	A0	CH-IN-	00.0 ►	00.1 ►	00.2 ►	00.3 ►	00.4 ►	00.5 ►
1	0	0	CH-OUT-	00.0	00.1	00.2	00.3	00.4	00.5
1	0	1	CH-OUT-	01.0	01.1	01.2	01.3	01.4	01.5
1	1	0	CH-OUT-	02.0	02.1	02.2	02.3	02.4	02.5
1	1	1	CH-OUT-	03.0	03.1	03.2	03.3	03.4	03.5
0	X	X	CH-OUT	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z

Operating sequence

ENA = 1

A1-A0 = "00"

CH-IN-00.0 ► CH-OUT-00.0
CH-IN-00.1 ► CH-OUT-00.1
CH-IN-00.2 ► CH-OUT-00.2
CH-IN-00.3 ► CH-OUT-00.3
CH-IN-00.4 ► CH-OUT-00.4
CH-IN-00.5 ► CH-OUT-00.5

A1-A0 = "01"

CH-IN-00.0 ► CH-OUT-01.0
CH-IN-00.1 ► CH-OUT-01.1
CH-IN-00.2 ► CH-OUT-01.2
CH-IN-00.3 ► CH-OUT-01.3
CH-IN-00.4 ► CH-OUT-01.4
CH-IN-00.5 ► CH-OUT-01.5

A1-A0 = "10"

CH-IN-00.0 ► CH-OUT-02.0
CH-IN-00.1 ► CH-OUT-02.1
CH-IN-00.2 ► CH-OUT-02.2
CH-IN-00.3 ► CH-OUT-02.3
CH-IN-00.4 ► CH-OUT-02.4
CH-IN-00.5 ► CH-OUT-02.5

A1-A0 = "11"

CH-IN-00.0 ► CH-OUT-03.0
CH-IN-00.1 ► CH-OUT-03.1
CH-IN-00.2 ► CH-OUT-03.2
CH-IN-00.3 ► CH-OUT-03.3
CH-IN-00.4 ► CH-OUT-03.4
CH-IN-00.5 ► CH-OUT-03.5

Connector pinout (aliases signals, top view)


Pin	Signal	Signal	Pin
01	CH-OUT-GND	CH-OUT-GND	40
02	CH-OUT-00.0	CH-OUT-02.0	39
03	CH-OUT-00.1	CH-OUT-02.1	38
04	CH-OUT-00.2	CH-OUT-02.2	37
05	CH-OUT-00.3	CH-OUT-02.3	36
06	CH-OUT-00.4	CH-OUT-02.4	35
07	CH-OUT-00.5	CH-OUT-02.5	34
08	CH-OUT-GND	CH-OUT-GND	33
09	CH-OUT-01.0	CH-OUT-03.0	32
10	CH-OUT-01.1	CH-OUT-03.1	31
11	CH-OUT-01.2	CH-OUT-03.2	30
12	CH-OUT-01.3	CH-OUT-03.3	29
13	CH-OUT-01.4	CH-OUT-03.4	28
14	CH-OUT-01.5	CH-OUT-03.5	27
15	CH-IN-00.0	A0	26
16	CH-IN-00.1	A1	25
17	CH-IN-00.2	ENA	24
18	CH-IN-00.3	GND (*)	23
19	CH-IN-00.4	GND (*)	22
20	CH-IN-00.5	Power	21

(*) GND at pins 22/23 is used for both Power GND and CH-IN-GND.


Using 8 NanoPlex NPS-06-01-04A units for a 32-channel system

The following diagram shows how 8 NanoPlex NPS-06-01-04A units can be used to create a massive, 32-channel ISP Programming multiplier. In this example, 8 input channels are from the output of any brand or type of ISP-Programming tool.

Example diagram 1/2

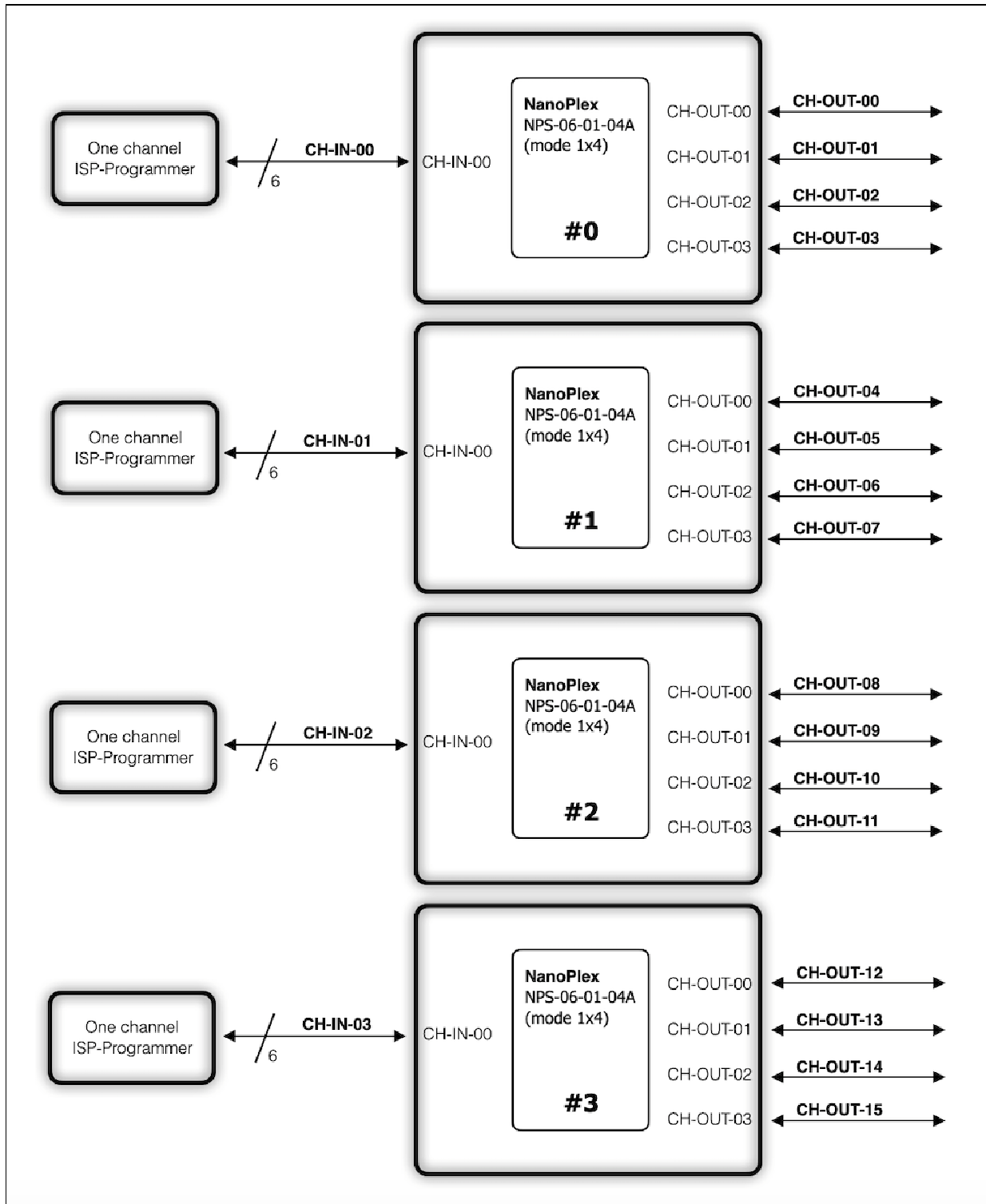

Example diagram 2/2

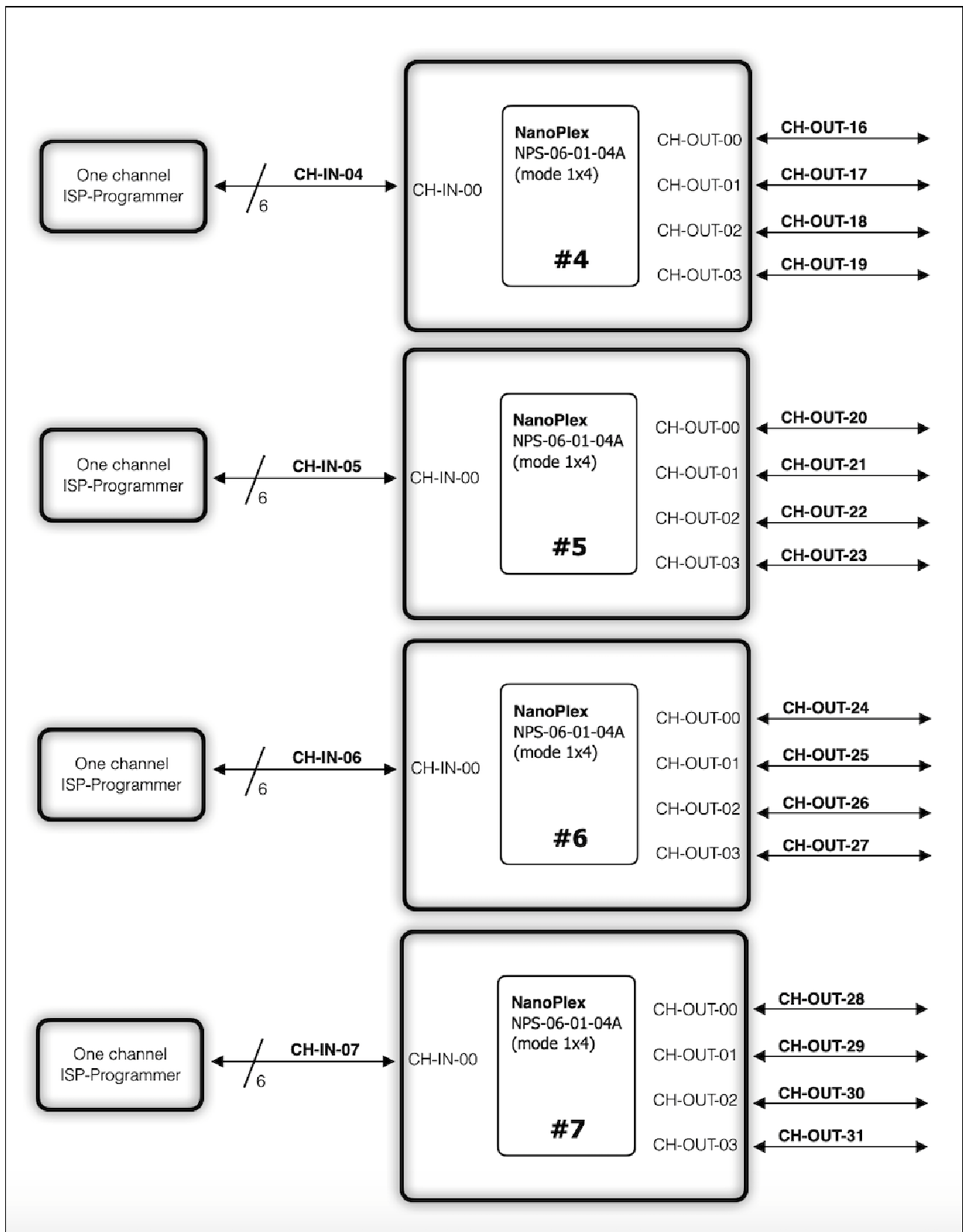


Channels and aliases

NanoPlex Unit	Input Channels		Input Aliases	Output Channels		Output Aliases
#0	CH-IN-00	►	CH-IN-00	CH-OUT-00	►	CH-OUT-00
#0				CH-OUT-01	►	CH-OUT-01
#0				CH-OUT-02	►	CH-OUT-02
#0				CH-OUT-03	►	CH-OUT-03
#1	CH-IN-00	►	CH-IN-01	CH-OUT-00	►	CH-OUT-04
#1				CH-OUT-01	►	CH-OUT-05
#1				CH-OUT-02	►	CH-OUT-06
#1				CH-OUT-03	►	CH-OUT-07
...
...
...
#7	CH-IN-00	►	CH-IN-07	CH-OUT-00	►	CH-OUT-28
#7				CH-OUT-01	►	CH-OUT-29
#7				CH-OUT-02	►	CH-OUT-30
#7				CH-OUT-03	►	CH-OUT-31

Mode 2x8

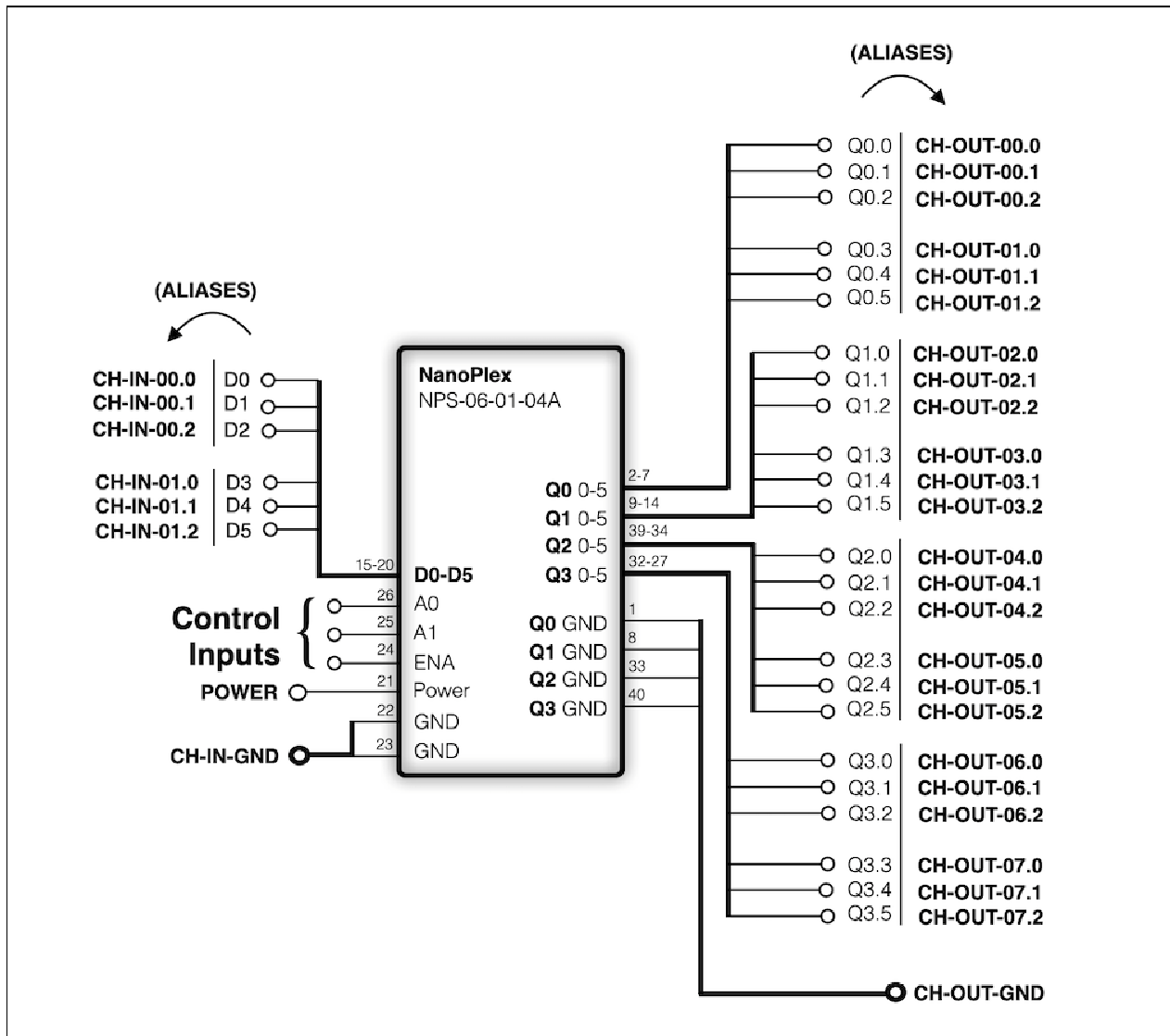3 Signals per channel
2 Input channels
8 Output channels



Truth table

(the symbol ► stands for "connected to")

ENA	A1	A0	CH-IN-	00.0 ►	00.1 ►	00.2 ►	01.0 ►	01.1 ►	01.2 ►
1	0	0	CH-OUT-	00.0	00.1	00.2	01.0	01.1	01.2
1	0	1	CH-OUT-	02.0	02.1	02.2	03.0	03.1	03.2
1	1	0	CH-OUT-	04.0	04.1	04.2	05.0	05.1	05.2
1	1	1	CH-OUT-	06.0	06.1	06.2	07.0	07.1	07.2
0	X	X	CH-OUT	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z

Operating sequence

ENA = 1

A1-A0 = "00"

CH-IN-00.0 ► CH-OUT-00.0
 CH-IN-00.1 ► CH-OUT-00.1
 CH-IN-00.2 ► CH-OUT-00.2
 CH-IN-01.0 ► CH-OUT-01.0
 CH-IN-01.1 ► CH-OUT-01.1
 CH-IN-01.2 ► CH-OUT-01.2

A1-A0 = "01"

CH-IN-00.0 ► CH-OUT-02.0
 CH-IN-00.1 ► CH-OUT-02.1
 CH-IN-00.2 ► CH-OUT-02.2
 CH-IN-01.0 ► CH-OUT-03.0
 CH-IN-01.1 ► CH-OUT-03.1
 CH-IN-01.2 ► CH-OUT-03.2

A1-A0 = "10"

CH-IN-00.0 ► CH-OUT-04.0
 CH-IN-00.1 ► CH-OUT-04.1
 CH-IN-00.2 ► CH-OUT-04.2
 CH-IN-01.0 ► CH-OUT-05.0
 CH-IN-01.1 ► CH-OUT-05.1
 CH-IN-01.2 ► CH-OUT-05.2

A1-A0 = "11"

CH-IN-00.0 ► CH-OUT-06.0
 CH-IN-00.1 ► CH-OUT-06.1
 CH-IN-00.2 ► CH-OUT-06.2
 CH-IN-01.0 ► CH-OUT-07.0
 CH-IN-01.1 ► CH-OUT-07.1
 CH-IN-01.2 ► CH-OUT-07.2

Connector pinout (aliases signals, top view)


Pin	Signal	Signal	Pin
01	CH-OUT-GND	CH-OUT-GND	40
02	CH-OUT-00.0	CH-OUT-04.0	39
03	CH-OUT-00.1	CH-OUT-04.1	38
04	CH-OUT-00.2	CH-OUT-04.2	37
05	CH-OUT-01.0	CH-OUT-05.0	36
06	CH-OUT-01.1	CH-OUT-05.1	35
07	CH-OUT-01.2	CH-OUT-05.2	34
08	CH-OUT-GND	CH-OUT-GND	33
09	CH-OUT-02.0	CH-OUT-06.0	32
10	CH-OUT-02.1	CH-OUT-06.1	31
11	CH-OUT-02.2	CH-OUT-06.2	30
12	CH-OUT-03.0	CH-OUT-07.0	29
13	CH-OUT-03.1	CH-OUT-07.1	28
14	CH-OUT-03.2	CH-OUT-07.2	27
15	CH-IN-00.0	A0	26
16	CH-IN-00.1	A1	25
17	CH-IN-00.2	ENA	24
18	CH-IN-01.0	GND (*)	23
19	CH-IN-01.1	GND (*)	22
20	CH-IN-01.2	Power	21

(*) GND at pins 22/23 is used for both Power GND and CH-IN-GND.


Using 8 NanoPlex NPS-06-01-04A units for a 64-channel system

The following diagram shows how 8 NanoPlex NPS-06-01-04A units can be used to create a massive, 64-channel ISP Programming multiplier. In this example, 16 input channels are from the output of any brand or type of ISP-Programming tool.

Example diagram 1/2

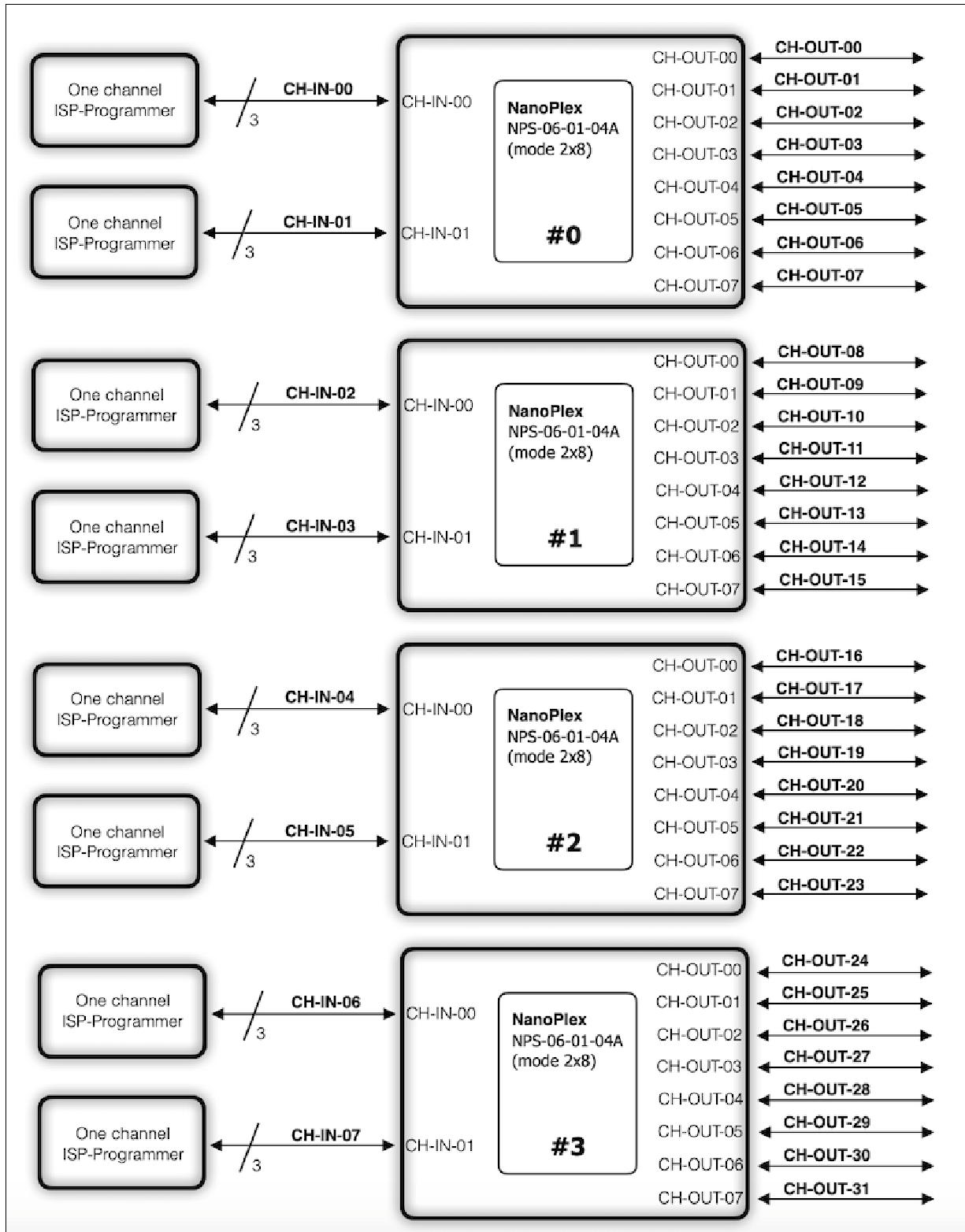

Example diagram 2/2

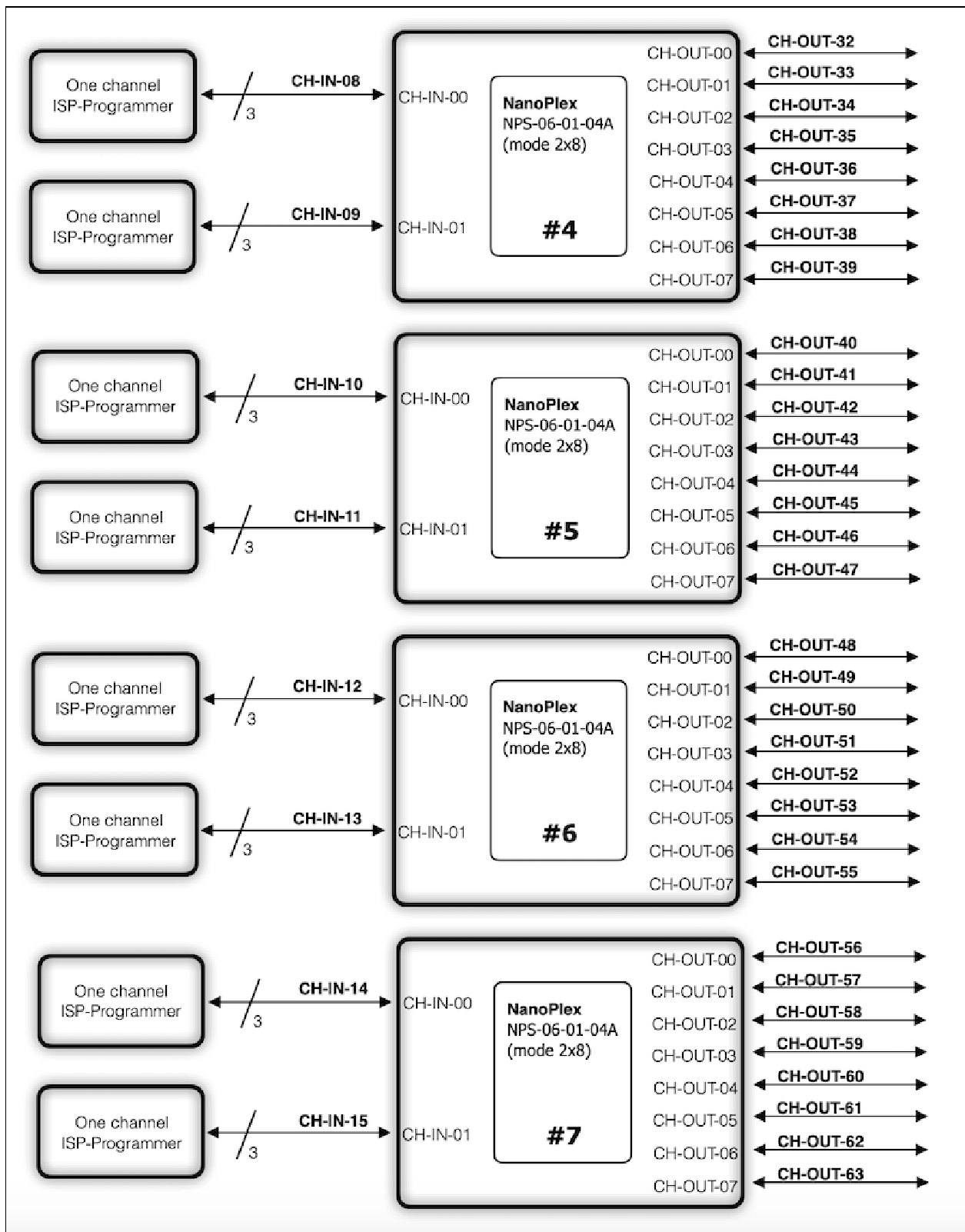

Channels and aliases


NanoPlex Unit	Input Channels		Input Aliases	Output Channels		Output Aliases
#0	CH-IN-00	►	CH-IN-00	CH-OUT-00	►	CH-OUT-00
#0				CH-OUT-01	►	CH-OUT-01
#0				CH-OUT-02	►	CH-OUT-02
#0				CH-OUT-03	►	CH-OUT-03
#0	CH-IN-01	►	CH-IN-01	CH-OUT-04	►	CH-OUT-04
#0				CH-OUT-05	►	CH-OUT-05
#0				CH-OUT-06	►	CH-OUT-06
#0				CH-OUT-07	►	CH-OUT-07
#1	CH-IN-00	►	CH-IN-02	CH-OUT-00	►	CH-OUT-08
#1				CH-OUT-01	►	CH-OUT-09
#1				CH-OUT-02	►	CH-OUT-10
#1				CH-OUT-03	►	CH-OUT-11
#1	CH-IN-01	►	CH-IN-03	CH-OUT-04	►	CH-OUT-12
#1				CH-OUT-05	►	CH-OUT-13
#1				CH-OUT-06	►	CH-OUT-14
#1				CH-OUT-07	►	CH-OUT-15
...
...
...
#7	CH-IN-00	►	CH-IN-14	CH-OUT-00	►	CH-OUT-56
#7				CH-OUT-01	►	CH-OUT-57
#7				CH-OUT-02	►	CH-OUT-58
#7				CH-OUT-03	►	CH-OUT-59
#7	CH-IN-01	►	CH-IN-15	CH-OUT-04	►	CH-OUT-60
#7				CH-OUT-05	►	CH-OUT-61
#7				CH-OUT-06	►	CH-OUT-62
#7				CH-OUT-07	►	CH-OUT-63

Mode 3x12

2 Signals per channel

3 Input channels

12 Output channels

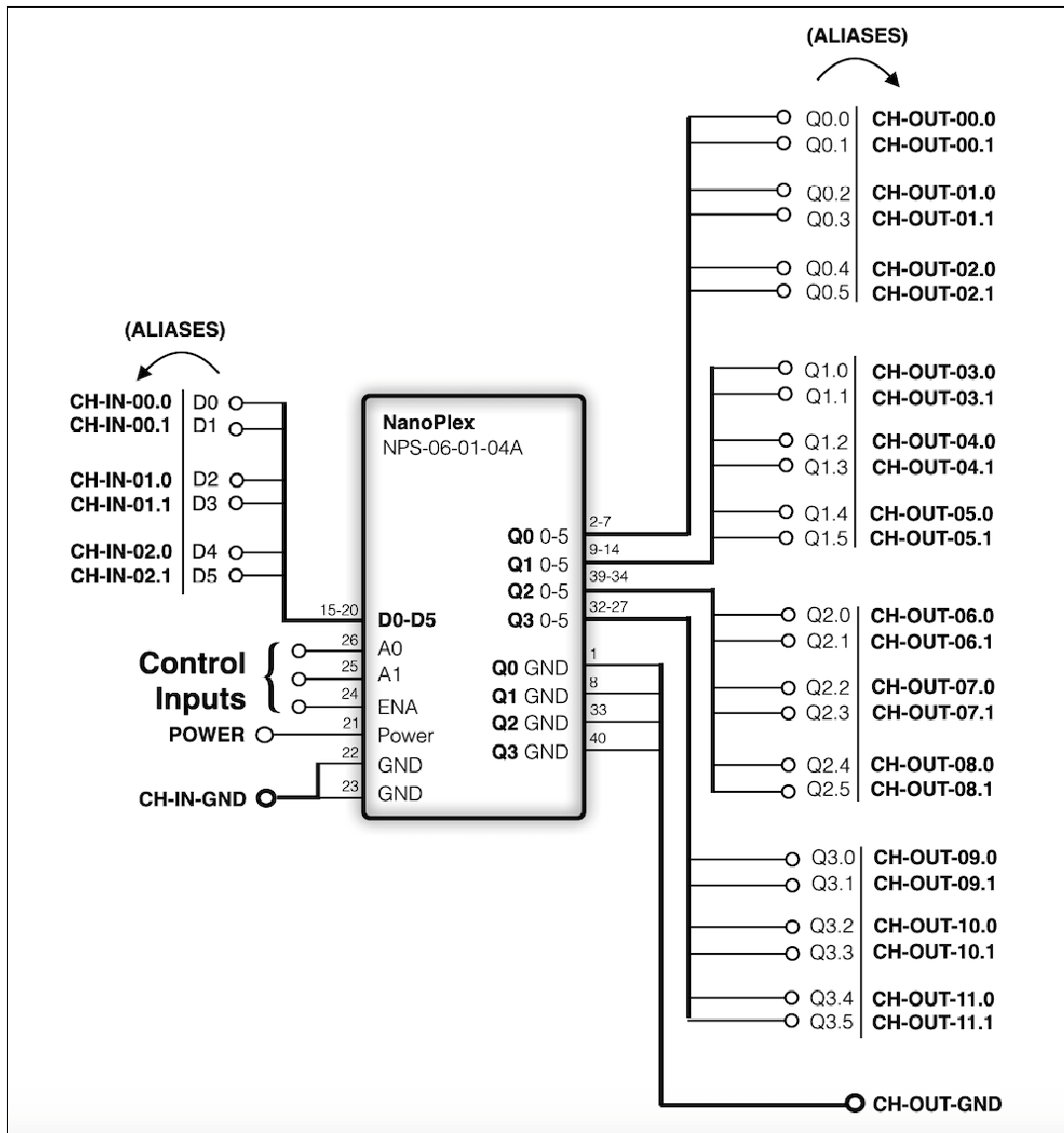

Truth table

(the symbol ► stands for “connected to”)

ENA	A1	A0	CH-IN-	00.0 ►	00.1 ►	01.0 ►	01.1 ►	02.0 ►	02.1 ►
1	0	0	CH-OUT-	00.0	00.1	01.0	01.1	02.0	02.1
1	0	1	CH-OUT-	03.0	03.1	04.0	04.1	05.0	05.1
1	1	0	CH-OUT-	06.0	06.1	07.0	07.1	08.0	08.1
1	1	1	CH-OUT-	09.0	09.1	10.0	10.1	11.0	11.1
0	X	X	CH-OUT	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z

Operating sequence

ENA = 1

A1-A0 = "00"

CH-IN-00.0 ► CH-OUT-00.0
 CH-IN-00.1 ► CH-OUT-00.1
 CH-IN-01.0 ► CH-OUT-01.0
 CH-IN-01.1 ► CH-OUT-01.1
 CH-IN-02.0 ► CH-OUT-02.0
 CH-IN-02.1 ► CH-OUT-02.1

A1-A0 = "01"

CH-IN-00.0 ► CH-OUT-03.0
 CH-IN-00.1 ► CH-OUT-03.1
 CH-IN-01.0 ► CH-OUT-04.0
 CH-IN-01.1 ► CH-OUT-04.1
 CH-IN-02.0 ► CH-OUT-05.0
 CH-IN-02.1 ► CH-OUT-05.1

A1-A0 = "10"

CH-IN-00.0 ► CH-OUT-06.0
 CH-IN-00.1 ► CH-OUT-06.1
 CH-IN-01.0 ► CH-OUT-07.0
 CH-IN-01.1 ► CH-OUT-07.1
 CH-IN-02.0 ► CH-OUT-08.0
 CH-IN-02.1 ► CH-OUT-08.1

A1-A0 = "11"

CH-IN-00.0 ► CH-OUT-09.0
 CH-IN-00.1 ► CH-OUT-09.1
 CH-IN-01.0 ► CH-OUT-10.0
 CH-IN-01.1 ► CH-OUT-10.1
 CH-IN-02.0 ► CH-OUT-11.0
 CH-IN-02.1 ► CH-OUT-11.1

Connector pinout (aliases signals, top view)

Pin	Signal
01	CH-OUT-GND
02	CH-OUT-00.0
03	CH-OUT-00.1
04	CH-OUT-01.0
05	CH-OUT-01.1
06	CH-OUT-02.0
07	CH-OUT-02.1
08	CH-OUT-GND
09	CH-OUT-03.0
10	CH-OUT-03.1
11	CH-OUT-04.0
12	CH-OUT-04.1
13	CH-OUT-05.0
14	CH-OUT-05.1
15	CH-IN-00.0
16	CH-IN-00.1
17	CH-IN-01.0
18	CH-IN-01.1
19	CH-IN-02.0
20	CH-IN-02.1


Signal	Pin
CH-OUT-GND	40
CH-OUT-06.0	39
CH-OUT-06.1	38
CH-OUT-07.2	37
CH-OUT-07.3	36
CH-OUT-08.4	35
CH-OUT-08.5	34
CH-OUT-GND	33
CH-OUT-09.0	32
CH-OUT-09.1	31
CH-OUT-10.0	30
CH-OUT-10.1	29
CH-OUT-11.0	28
CH-OUT-11.1	27
A0	26
A1	25
ENA	24
GND (*)	23
GND (*)	22
Power	21

(*) GND at pins 22/23 is used for both Power GND and CH-IN-GND.

Using 4 NanoPlex NPS-06-01-04A units for a 48-channel system

The following diagram shows how 4 NanoPlex NPS-06-01-04A units can be used to create a massive, 48-channel ISP Programming multiplier. In this example, 12 input channels are from the output of any brand or type of ISP-Programming tool.

Example diagram

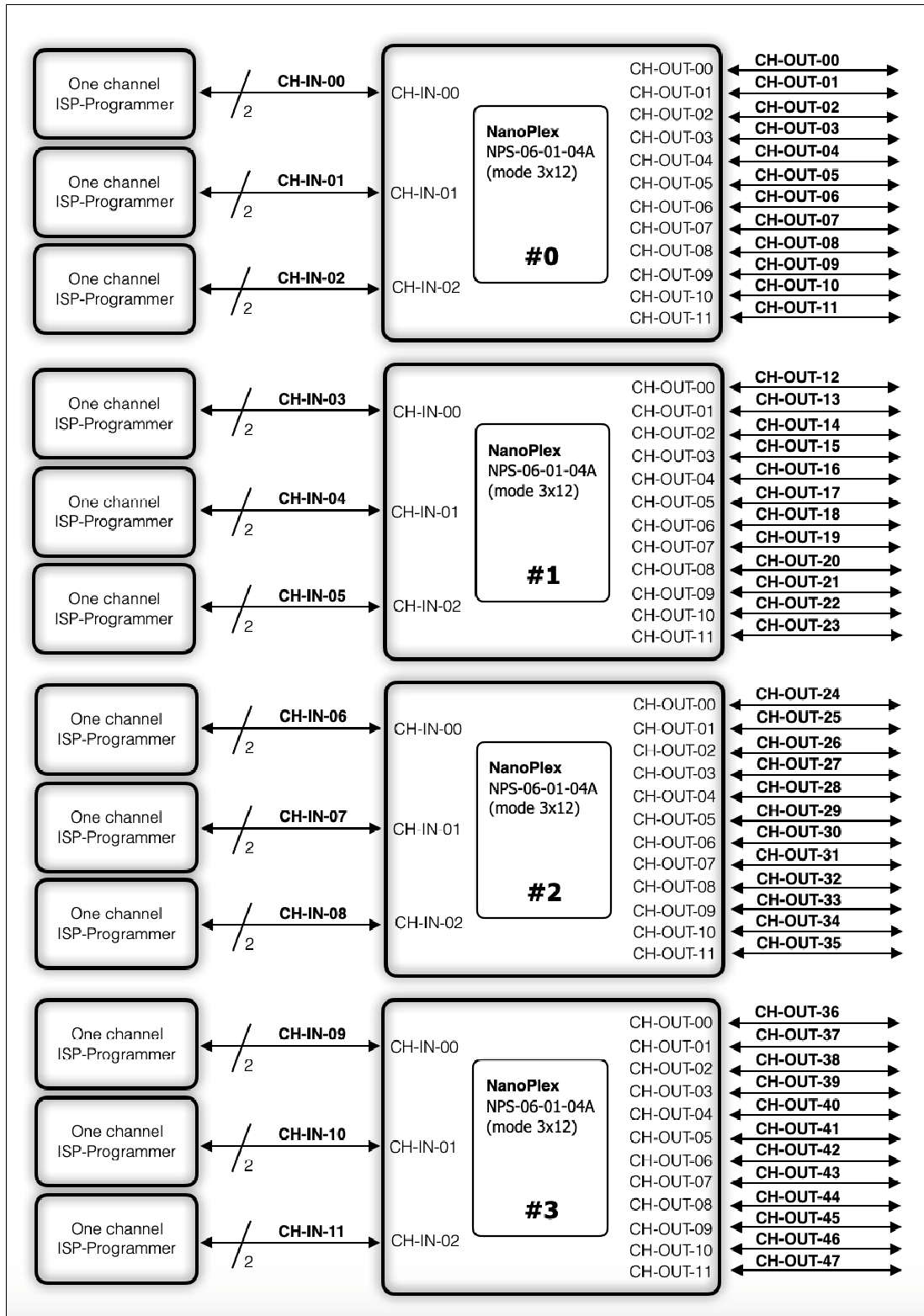


Channels and aliases

NanoPlex Unit	Input Channels		Input Aliases	Output Channels		Output Aliases
#0	CH-IN-00	►	CH-IN-00	CH-OUT-00	►	CH-OUT-00
#0				CH-OUT-01	►	CH-OUT-01
#0				CH-OUT-02	►	CH-OUT-02
#0				CH-OUT-03	►	CH-OUT-03
#0	CH-IN-01	►	CH-IN-01	CH-OUT-04	►	CH-OUT-04
#0				CH-OUT-05	►	CH-OUT-05
#0				CH-OUT-06	►	CH-OUT-06
#0				CH-OUT-07	►	CH-OUT-07
#0	CH-IN-02	►	CH-IN-02	CH-OUT-08	►	CH-OUT-08
#0				CH-OUT-09	►	CH-OUT-09
#0				CH-OUT-10	►	CH-OUT-10
#0				CH-OUT-11	►	CH-OUT-11
#1	CH-IN-00	►	CH-IN-03	CH-OUT-00	►	CH-OUT-12
#1				CH-OUT-01	►	CH-OUT-13
#1				CH-OUT-02	►	CH-OUT-14
#1				CH-OUT-03	►	CH-OUT-15
#1	CH-IN-01	►	CH-IN-04	CH-OUT-04	►	CH-OUT-16
#1				CH-OUT-05	►	CH-OUT-17
#1				CH-OUT-06	►	CH-OUT-18
#1				CH-OUT-07	►	CH-OUT-19
#1	CH-IN-02	►	CH-IN-05	CH-OUT-08	►	CH-OUT-20
#1				CH-OUT-09	►	CH-OUT-21
#1				CH-OUT-10	►	CH-OUT-22
#1				CH-OUT-11	►	CH-OUT-23
...
...
...
#3	CH-IN-00	►	CH-IN-09	CH-OUT-00	►	CH-OUT-36
#3				CH-OUT-01	►	CH-OUT-37
#3				CH-OUT-02	►	CH-OUT-38
#3				CH-OUT-03	►	CH-OUT-39
#3	CH-IN-01	►	CH-IN-10	CH-OUT-04	►	CH-OUT-40
#3				CH-OUT-05	►	CH-OUT-41
#3				CH-OUT-06	►	CH-OUT-42
#3				CH-OUT-07	►	CH-OUT-43
#3	CH-IN-02	►	CH-IN-11	CH-OUT-08	►	CH-OUT-44
#3				CH-OUT-09	►	CH-OUT-45
#3				CH-OUT-10	►	CH-OUT-46
#3				CH-OUT-11	►	CH-OUT-47

Mode 6x24

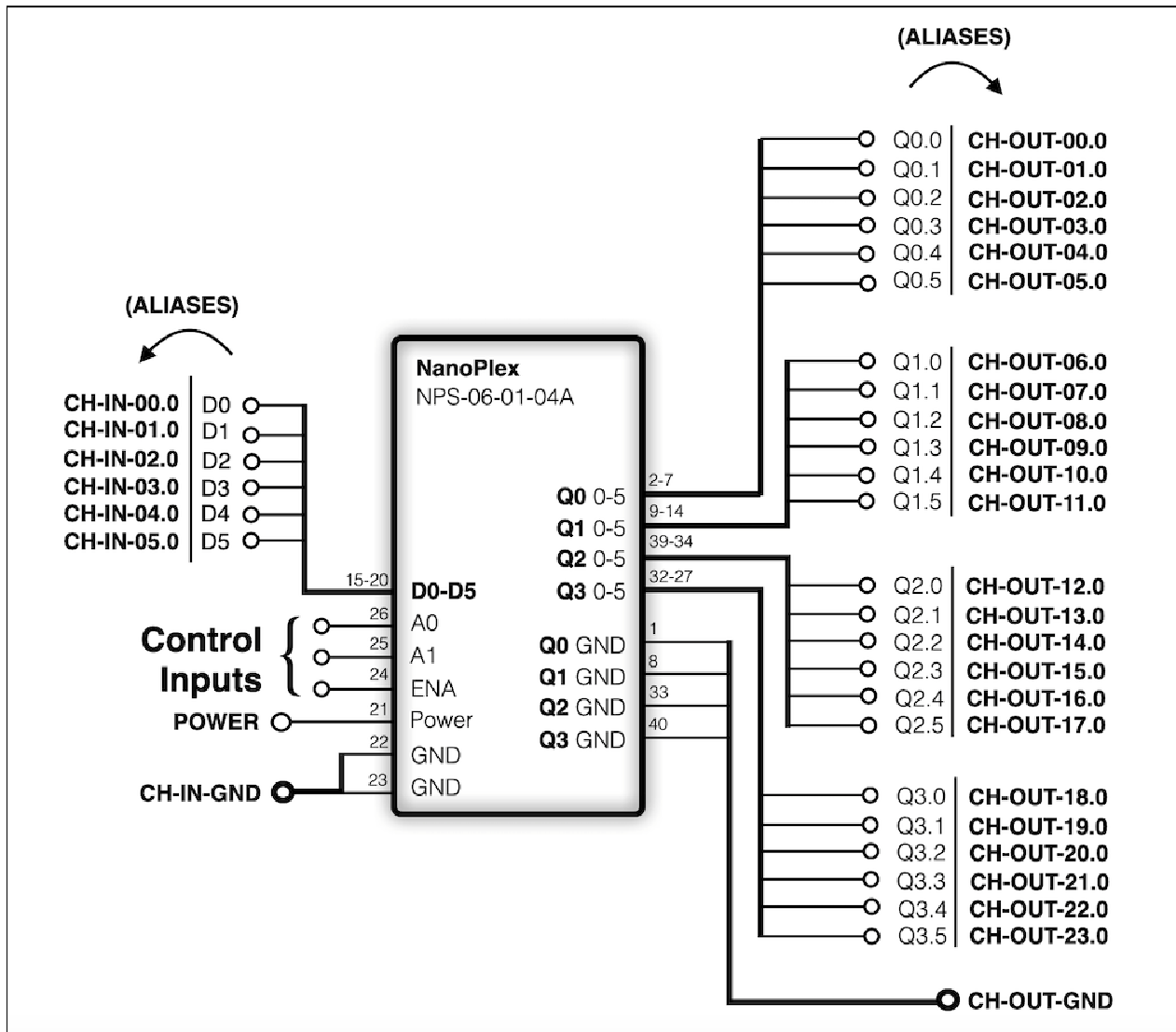1 Signals per channel
6 Input channels
24 Output channels



Truth table

(the symbol ► stands for "connected to")

ENA	A1	A0	CH-IN-	00.0 ►	01.0 ►	02.0 ►	03.0 ►	04.0 ►	05.0 ►
1	0	0	CH-OUT-	00.0	01.0	02.0	03.0	04.0	05.0
1	0	1	CH-OUT-	06.0	07.0	08.0	09.0	10.0	11.0
1	1	0	CH-OUT-	12.0	13.0	14.0	15.0	16.0	17.0
1	1	1	CH-OUT-	18.0	19.0	20.0	21.0	22.0	23.0
0	X	X	CH-OUT	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z	HI-Z

Operating sequence

ENA = 1

A1-A0 = "00"

CH-IN-00.0 ► CH-OUT-00.0
 CH-IN-01.0 ► CH-OUT-01.0
 CH-IN-02.0 ► CH-OUT-02.0
 CH-IN-03.0 ► CH-OUT-03.0
 CH-IN-04.0 ► CH-OUT-04.0
 CH-IN-05.0 ► CH-OUT-05.0

A1-A0 = "01"

CH-IN-00.0 ► CH-OUT-06.0
 CH-IN-01.0 ► CH-OUT-07.0
 CH-IN-02.0 ► CH-OUT-08.0
 CH-IN-03.0 ► CH-OUT-09.0
 CH-IN-04.0 ► CH-OUT-10.0
 CH-IN-05.0 ► CH-OUT-11.0

A1-A0 = "10"

CH-IN-00.0 ► CH-OUT-12.0
 CH-IN-01.0 ► CH-OUT-13.0
 CH-IN-02.0 ► CH-OUT-14.0
 CH-IN-03.0 ► CH-OUT-15.0
 CH-IN-04.0 ► CH-OUT-16.0
 CH-IN-05.0 ► CH-OUT-17.0

A1-A0 = "11"

CH-IN-00.0 ► CH-OUT-18.0
 CH-IN-01.0 ► CH-OUT-19.0
 CH-IN-02.0 ► CH-OUT-20.0
 CH-IN-03.0 ► CH-OUT-21.0
 CH-IN-04.0 ► CH-OUT-22.0
 CH-IN-05.0 ► CH-OUT-23.0

Connector pinout (aliases signals, top view)

Pin	Signal	Signal	Pin
01	CH-OUT-GND	CH-OUT-GND	40
02	CH-OUT-00.0	CH-OUT-12.0	39
03	CH-OUT-01.0	CH-OUT-13.0	38
04	CH-OUT-02.0	CH-OUT-14.0	37
05	CH-OUT-03.0	CH-OUT-15.0	36
06	CH-OUT-04.0	CH-OUT-16.0	35
07	CH-OUT-05.0	CH-OUT-17.0	34
08	CH-OUT-GND	CH-OUT-GND	33
09	CH-OUT-06.0	CH-OUT-18.0	32
10	CH-OUT-07.0	CH-OUT-19.0	31
11	CH-OUT-08.0	CH-OUT-20.0	30
12	CH-OUT-09.0	CH-OUT-21.0	29
13	CH-OUT-10.0	CH-OUT-22.0	28
14	CH-OUT-11.0	CH-OUT-23.0	27
15	CH-IN-00.0	A0	26
16	CH-IN-01.0	A1	25
17	CH-IN-02.0	ENA	24
18	CH-IN-03.0	GND (*)	23
19	CH-IN-04.0	GND (*)	22
20	CH-IN-05.0	Power	21

(*) GND at pins 22/23 is used for both Power GND and CH-IN-GND.

About Manta Systems

Manta Systems is a high-tech company, global leader in high-density signal switching for In-System Programming (ISP) and Testing Systems. The company targets the electronic boards assembly market, where a high number of connections is required. Manta Systems flagship product is NanoPlex™, a series of Channels Multipliers for In-System Programming (ISP) and Testing instruments. NanoPlex is the **world's first universal tool** providing end-user with the possibility of having compact, easy-to-use, professional, reliable In-System Programming (ISP) and Testing Channel Multiplication functionality.

Warranty

All Manta Systems products are covered by a **three-year warranty** against defects and workmanship from the purchase date. The warranty only covers products when properly installed and used.

Orders

All NanoPlex™ Series products are generally **off-the-shelf**.

Shipping is within **24 hours** from order reception.

Free shipping & 30-day money back guarantee.

Disclaimer

Manta Systems is the owner of NanoPlex™ tradename. Manta Systems reserves the right to make improvements to NanoPlex™ Series and its documentation without notice. Information in this document is intended to be accurate and reliable. However, Manta Systems assumes no responsibility for its use; nor for any infringements of rights of third parties which may result from its use.

MANTA SYSTEMS WILL NOT BE LIABLE FOR DAMAGES RESULTING FROM LOSS OF DATA, PROFITS, USE OF PRODUCTS, OR INCIDENTAL OR CONSEQUENTIAL DAMAGES, EVEN IF ADVISED OF THE POSSIBILITY THEREOF.

Copyright © Manta Systems. All rights reserved.

NanoPlex™ is a tradename of Manta Systems.

All other product or service names are the property of their respective owners.

www.mantasys.com

info@mantasys.com

